

CARRY LOOK AHEAD ADDER ARCHITECTURE


$$G = AB, P = A \oplus B$$

$$C_{out} = G_0 + P_0 C_{in}, C_1 = G_1 + P_1 C_0$$


$$\longrightarrow C_1 = G_1 + P_1 G_0 + P_1 P_0 C_{in}$$

$$\longrightarrow C_N = G_N + P_N G_{N-1} + P_N P_{N-1} G_{N-2} + \dots + P_N P_{N-1} P_{N-2} \dots P_0 C_{in}$$
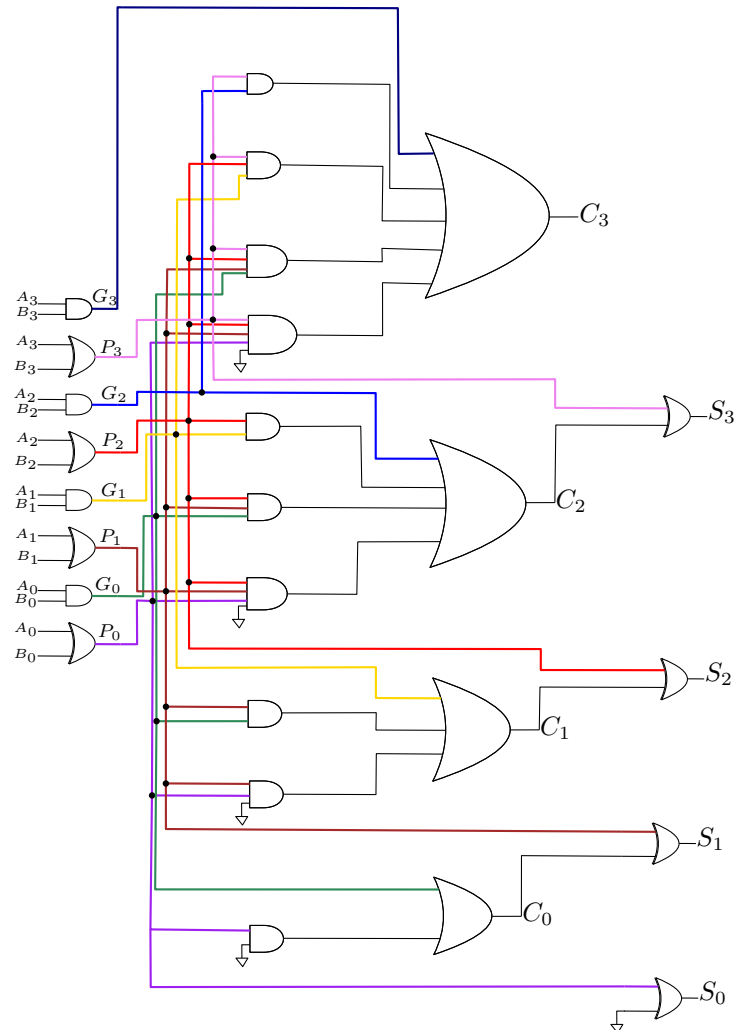
$$\longrightarrow C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_{in}$$



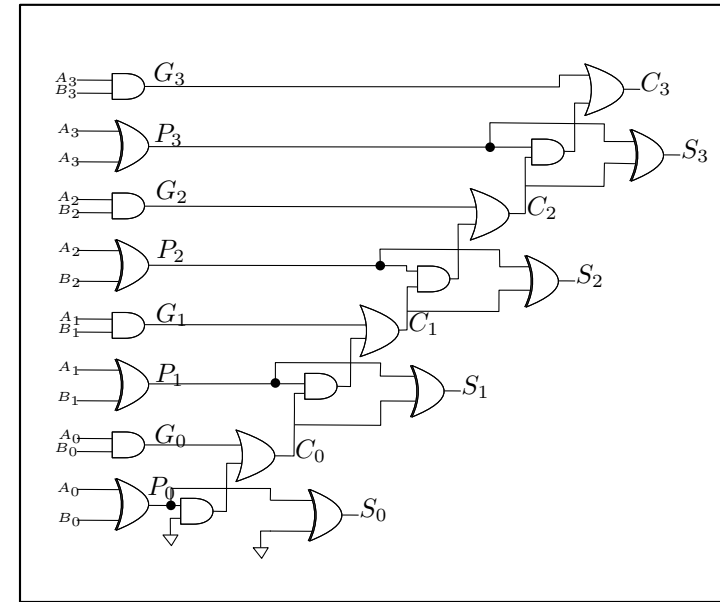4-bit CLA architecture takes 3 levels to generate C_{out} , and 4-levels to generate S.



4-bit RCA architecture takes 9 levels to generate C_{out} , and 8-levels to generate S.

■ P_0
■ P_1
■ P_2
■ P_3
■ G_0
■ G_1
■ G_2
■ G_3